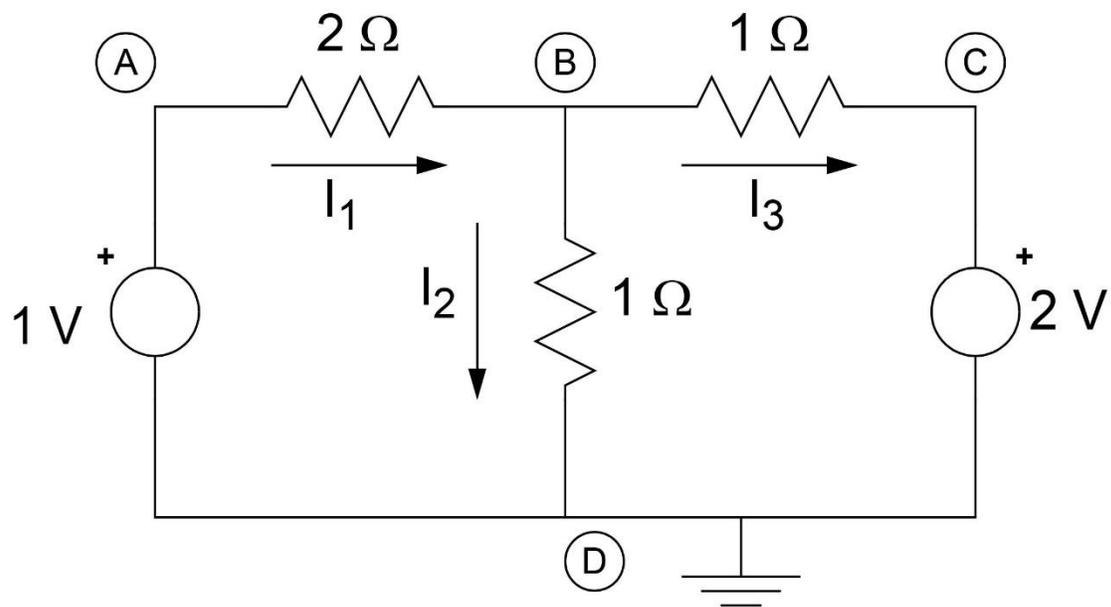


Quizzes for Module 9

Unit 9.1.2

Q 9.1.2.1: For the circuit shown below use superposition to calculate the currents I_1 , I_2 and I_3 when:

1. Only the 1 V source is turned ON and the other source is turned OFF.
2. Only the 2 V source is turned ON and the other source is turned OFF.
3. Calculate the currents when both voltage sources are turned ON.





Solution: (Self Assessment)

1. When 1V source turned ON: $I_1 = 0.4$ A, $I_2 = 0.2$ A and $I_3 = 0.2$ A.
2. When 2V source turned ON: $I_1 = -0.4$ A, $I_2 = 0.8$ A and $I_3 = -1.2$ A.
3. When both voltage sources are turned ON: $I_1 = 0$ A, $I_2 = 1$ A and $I_3 = -1$ A.


Unit 9.3.4

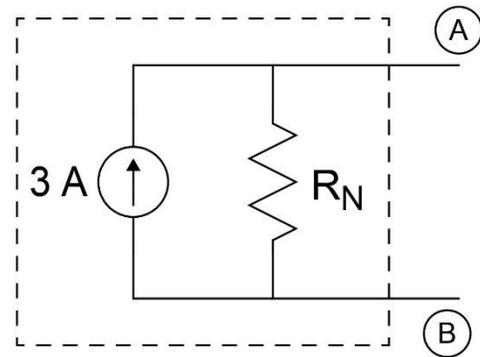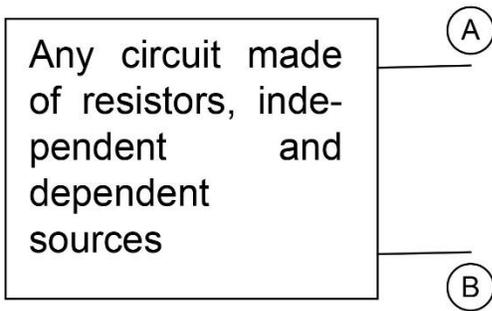Q 9.3.4.1: For the circuits shown below, the right circuit is the Norton equivalent of the circuit on the left. If the open-circuit voltage $V_{AB} = 10 \text{ V}$, then calculate the Norton resistance R_N .




Solution: (Self Assessment) The Norton resistance $R_N = 3.3333 \text{ ohms}$.

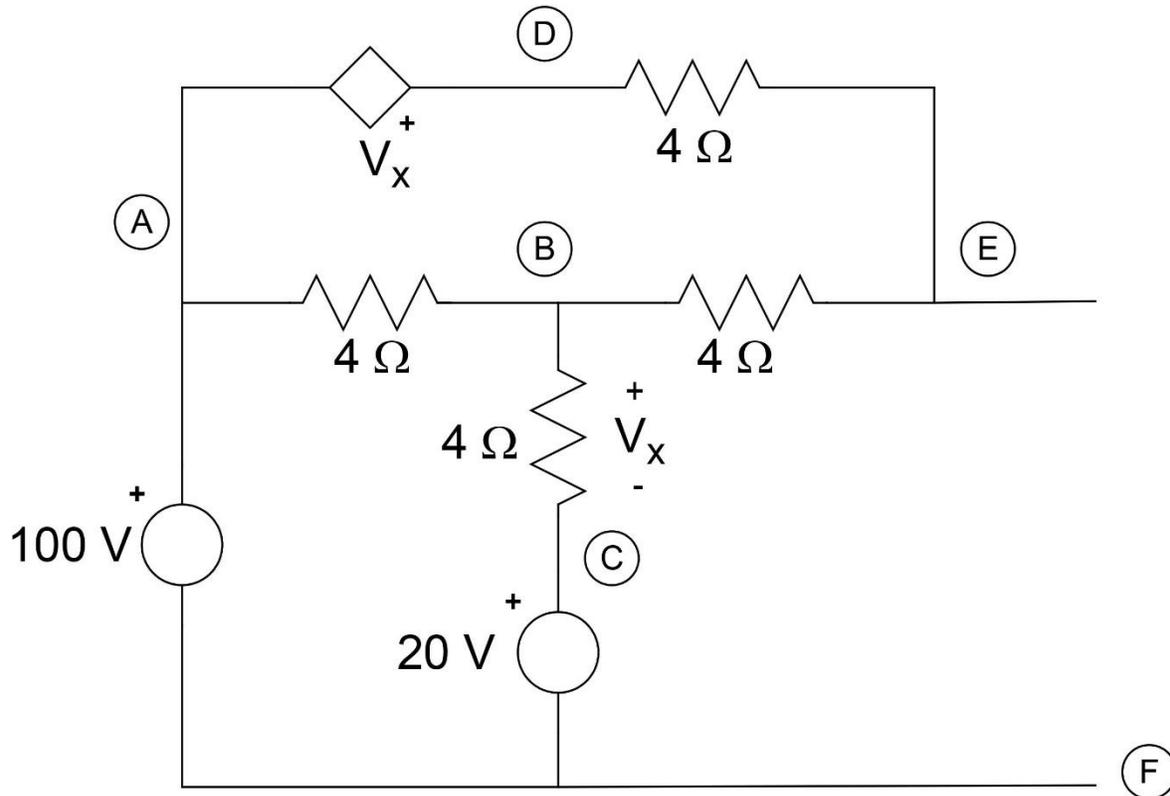Q 9.3.4.2: For the circuit shown below, calculate the open-circuit Thevenin voltage V_{EF} between the terminals E and F.




Solution: (Self Assessment) The open-circuit voltage $V_{EF} = 120$ V.

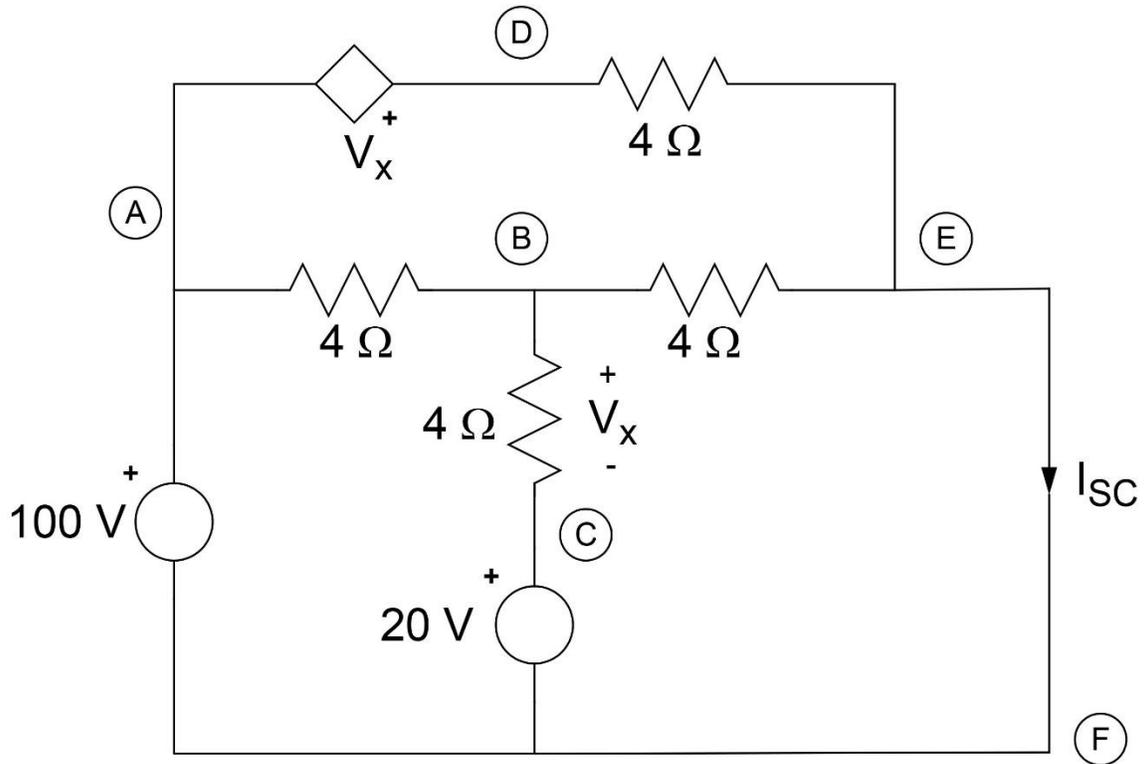Q 9.3.4.3: For the circuit shown below, calculate the short circuit current I_{SC} between the terminals E and F.



Solution: (Self Assessment) The short-circuit current $I_{sc} = 40$ A.

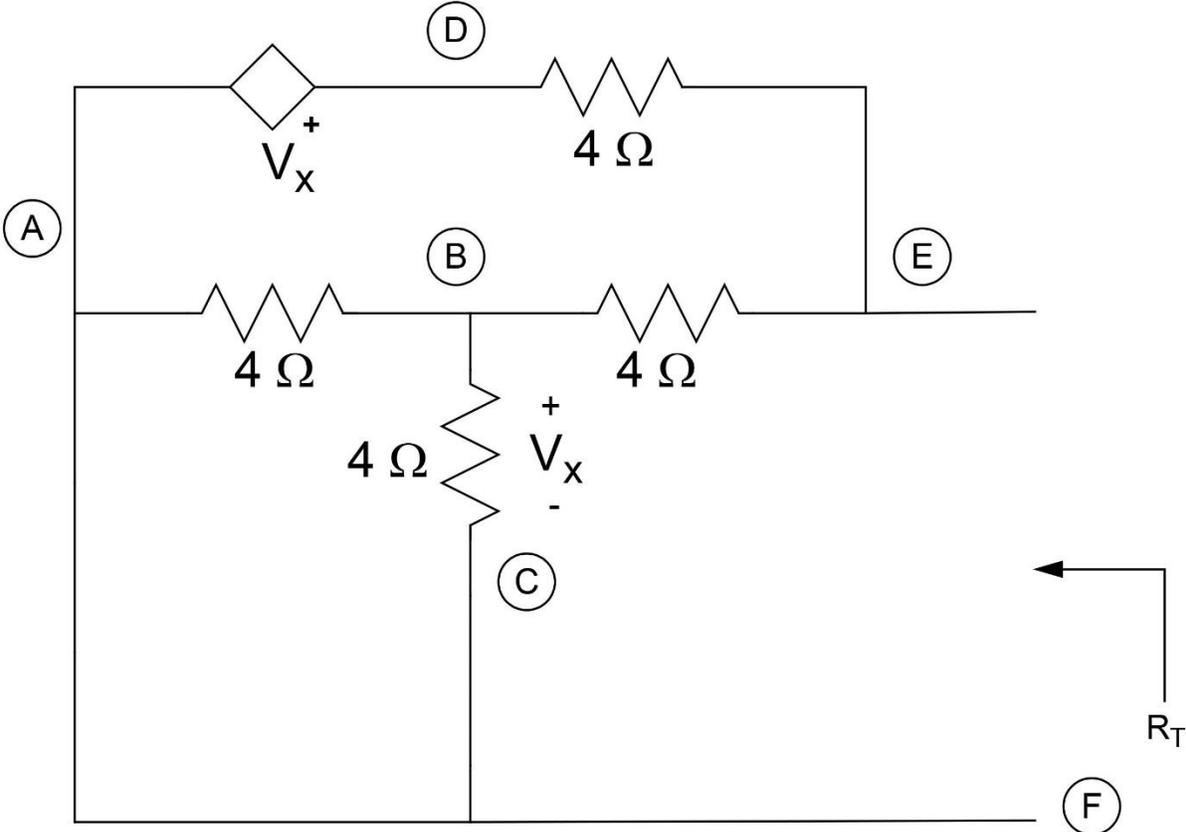Q 9.3.4.4: For the circuit shown below, calculate the input resistance R_T between the terminals E and F.



Solution: (Self Assessment) The input resistance $R_T = 3$ ohms.